



**ENGN 4213/6213 Digital Systems and Microprocessors**  
Semester 1, 2023

**Tutorial 3 – Worked Solutions**

**Question 1:**

Consider the following Verilog code when answering Question 1:

```
module mymod(  
    input wire a,  
    input wire b,  
    input wire f,  
    input wire [3:0] e,  
    output wire c);
```

```
    reg [3:0] d;
```


```
    always @(posedge b) begin  
        if(a) d <= e;  
        else if(f) d <= {1'b0, d[3:1]};  
    end
```

```
    assign c = d[0];
```

```
endmodule
```

↳ eg.  $d = 1101$   
↓  
 $d = 0110$   
↑  
 $1'b0$   $d[3:1]$

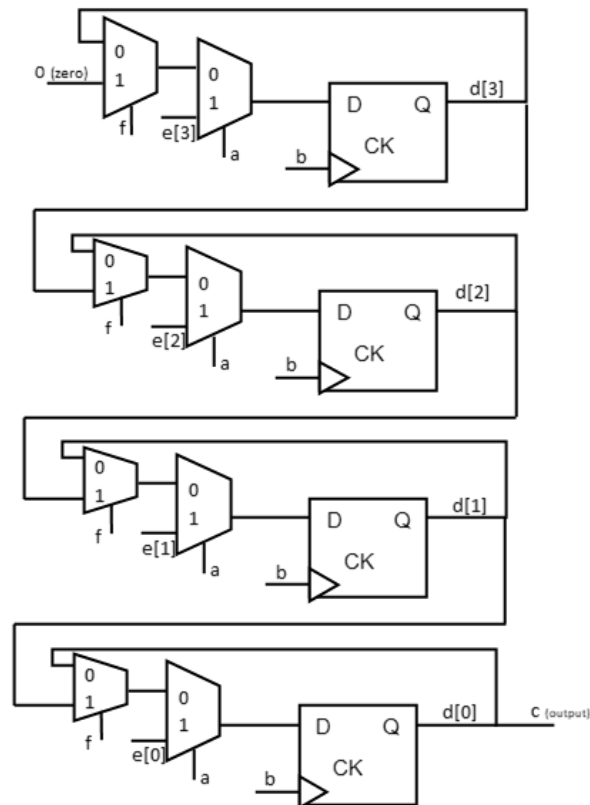a. Draw a block diagram detailed to flip-flop level



b. Explain the functional role of entities a, b, c, d, e and f

a is a mux selector signal. It can also be called a “parallel write-enable”, “parallel load”, or similarly named

b is the clock or edge trigger for the register

c is the output, also called serial output or lsb of the register

d is the storage register, also called bank of flipflops

e is the input data, also called parallel input

f is a mux selector signal, can also be called a “push” signal, which serves to shift data along the chain of flipflops

c. Suggest a possible use for the behaviour of this module

PISO shift register

d. Is this design sequential or combinational? Explain your answer

It is sequential since it has memory / timed behaviour.

e. Is this design synchronous or asynchronous? Explain your answer

It is synchronous since all flipflops are driven by the same clock.

## Question 2:

You wish to design a circuit with one button and four LEDs such that one LED is on at once, and each press of the button turns the next on the next LED in sequence:


 


Figure 1

a. What is the name of this type of counter?

One-hot counter: there are  $n$  outputs to the device, each delivering a "1" output for one clock cycle only in a rotating fashion

 b. Sketch the logic that might be used to implement this behaviour



Q: How to initialize bits in the register?  
 A: Could use similar design in Q1, i.e., write enable.  
 ...  
 in —> [reg] —> a

c. The output of this circuit can be used as a 'selector' for down-stream behaviour.

Write a short combinational Verilog snippet that takes the outputs of this counter as inputs, and has the following outputs itself:

- A 16-bit bus called  $A$
- An 8-bit bus called  $D$
- A one-bit line called  $LA$
- A one-bit line called  $RW$

 


Figure 2

The Verilog code should represent a design which does the following in order:

First state: Set A to '143' (the rest should be '0')

Second state: Set LA to '1'

Third state: Set D to '42', RW to '1', LA to '0'

Fourth state: Set RW to '0'

Congratulations, you just wrote your first state machine! This example would be suitable for storing the value '42' at address '143' in some external RAM.

```
module output_logic(
input wire in1, in2, in3, in4,
output reg [15:0] a,
output reg [7:0] d,
output reg rw,
output reg la);

    always @ (*) begin
        if(in1) begin
            a = 16'd143;
            d = 8'h00;
            rw = 1'b0;
            la = 1'b0;
        end
        else if (in2) begin
            a = 16'd143;
            d = 8'h00;
            rw = 1'b0;
            la = 1'b1;
        end
        else if (in3) begin
            a = 16'd143;
            d = 8'd42;
            rw = 1'b1;
            la = 1'b0;
        end
        else begin // equiv if(in4)
            a = 16'd143;
            d = 8'd42;
            rw = 1'b0;
            la = 1'b0;
        end
    end
end
endmodule
```