



**ENGN 4213/6213 Digital Systems and Microprocessors**  
Semester 1, 2023

**Tutorial 4**

**Question 1:**

- Describe the difference between a **Mealy** and a **Moore** machine showing a block diagram for each with the three key blocks and their inputs/outputs. Also, give a simple example for both.
- Why do Mealy machines have possible asynchronous outputs (unlike Moore machines) and how can we solve this (i.e. having synchronous outputs)?
- Why might someone choose to encode FSM states as binary, gray, or one-hot? What would the advantages and disadvantages of each be?
- What input and state should every FSM design have in order for the user to come back to a “safe” and known behaviour?

**Question 2:**

For this question, follow the order given below to develop a Finite State Machine:

- Determine the inputs/outputs and the required number of states
- Draw a state diagram
- Make a next state table, transition table, and output table

Design an FSM to simply transmit a HIGH pulse with a duration of only one clock cycle when some manual button is pressed and won't transmit another pulse until the button is released and pressed again.

**Question 3:**

In this question we practice designing a complex multi-module pin-code door access system that is controlled by a state machine. Based on the information and module instantiation provided below, complete the block diagram with the appropriate module name and module input/output.

- Given a very simple keypad (with the keys 0 and 1), the user is to enter an 8-digit code, which is compared with a list of valid pin codes held in the system's memory.
- If the pin is found amongst the valid codes, access is granted and the door may be opened. Once the door is shut again, the system will wait for a new pin input.
- If the pin entered by the user is not valid, access will not be granted; the system will reset and wait for a new input.
- Buttons A and B represent the 0 and 1 keys, there is also a reset button to cancel inputting a pin if a mistake has been made. Buttons must be debounced where required.
- As each keystroke is entered, a LED should light up indicating how many keystrokes have been entered (i.e., 8 LEDs light up when a full pin has been entered).
- If access is granted, a particular LED combination should indicate this (e.g. having every second LED on).
- The door could be represented by one of the sliding switches. As the door is unlocked by the

system, it must be opened (switch up) and closed again (switch back down) for the system to be reset.

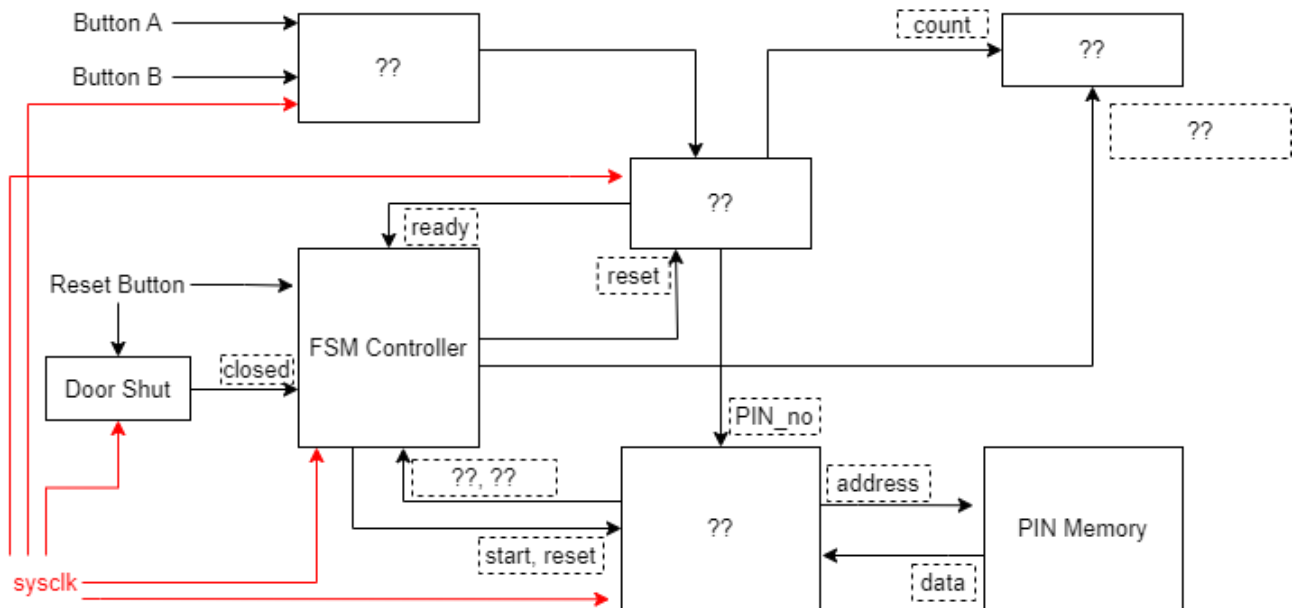


Figure 1 Block diagram of the door access system

```

module fsm_controller(
    input wire sysclk,
    input wire ready,
    input wire done,
    input wire closed_fsm,
    input wire found,
    input wire reset_btn,
    output reg start,
    output reg reset,
    output reg acc_gran);

module doubledebounce (
    input wire X0,
    input wire X1,
    input wire sysclk,
    input wire reset,
    output wire X0_deb,
    output wire X1_deb //X0 represents the input for the "0" key, X1 for
    //the "1" key
);

module keyproc(
    input wire X0_deb,
    input wire X1_deb,
    input wire reset,
    input wire sysclk,
    output wire ready,
    output reg [3:0] count,
    output reg [7:0] pin_password);

module LEDproc(

```

```

        input wire [3:0] count,
        input wire acc_grant,
        output reg [7:0] LEDS);

module PIN_memory (
    input wire [3:0] addr,
    output reg [7:0] data);

module pincomp(
    input wire start,
    input wire [7:0] pin_code,
    input wire [7:0] data,
    input wire sysclk,
    input wire reset,
    output reg [3:0] addr,
    output wire done,
    output wire found);

module doorshut(
    input wire reset,
    input wire closed_sw,
    input wire sysclk,
    output wire closed_fsm);

```