

Video Lecture 1

Non-ideal Behaviour

ENGN 4213/6213

Digital Systems and Microprocessors

What's in this lecture

- The operation of CMOS logic in nonideal conditions or under a load
- Timing and timing hazards


Resources

- Wakerly (5th edition) 14.3 and 14.4 for static and dynamic electrical behaviour of CMOS
(we do not get into as much detail as the book does)
- Wakerly 4.2 on circuit timing and 3.4 on timing hazards

On MOSFET/CMOS again

- We remember the following key characteristics
 - MOSFET transistors, when conducting, either behave as a *resistor* (“ohmic” or “triode” mode) or a *current source* (saturation mode), depending on the value of V_{GS} w.r.t. V_{DS}
 - CMOS technology combines n-MOS and p-MOS transistors
 - CMOS components use very little power if no logic switching occurs
 - CMOS logic relies on input/output signals being very close to the upper/lower reference voltages (e.g., 0V/5V)



The CMOS inverter

 

Inverter
Truth Table




IN	OUT
1	0
0	1

  

CMOS with nonideal input

Normal operation

 


$$I_w = 5V / (R_p + R_n) = 5V / (1.0002M\Omega) < 1\mu A$$

$$P_w = 5V \cdot I_w = 5\mu W$$

$$V_{out} = 5V - (200\Omega \cdot 1\mu A) = 4.9998V$$

Nonideal input

 


$$I_w = 5V / (2.8k\Omega) = 1.79mA$$

$$P_w = 5V \cdot I_w = 8.93mW$$

$$V_{out} = 5V - (800\Omega \cdot 1.79mA) = 3.57V$$

CMOS with resistive load


Acceptable load

 

$$I_{out} \approx 5V / (R_p + R_{load}) = 5V / (1.7k\Omega) = 3mA$$

$$V_{out} = 5V - (200\Omega \cdot 3mA) = 4.4V$$

Unacceptable load

 


$$I_{out} \approx 5V / (R_p + R_{load}) = 5V / (1.2k\Omega) = 4.16mA$$

$$V_{out} = 5V - (200\Omega \cdot 4.16mA) = 4.17V$$


CMOS with a capacitive load

 - Capacitive loads are always present.
 - Even the input terminal of a downstream logic stage has capacitance



The charging/discharging of the load capacitance **is not instantaneous**.

 The behaviour can be approximated as a **simple RC network** with a *rise/fall time*




Capacitance can have a big **impact on transition times and delays**.


You will solve a similar exercise in tutorial 1

Visualising some concepts

Will the propagation times be different?

 


 Which schematic is likely to produce the most heat?




Timing

 - We have seen that **load** and **logic complexity** can affect transition times
- It is common to have different propagation delays depending on the signal's pathway.
 - For example, in the circuit below, a change in input Z will show at the output after 1 gate has transitioned, while a change in Y will show after 2 transitions; X after 3 transitions.



Timing (2)

 
- This uncertainty in the switching timing of the output is reflected in **timing diagrams**. These are a graphical representation which can be useful to the designer in planning/refining a circuit design.
- **Simulation softwares** can be used to generate timing diagrams and you will learn how to do so during the labs.



- A good design should be expected to function for all input combinations. Therefore, considering **worst-case or maximum delays** is a safe way to ensure that the system will deliver dependable performance.


Hazards

- In some cases paths with different propagation delays can create *hazards*. In purely combinational circuits, these should be avoided.
 - **A hazard is a temporary “glitch” or incorrect output displayed as part of a transition in the circuit.** Since combinational circuits (unlike sequential ones, which we will discuss shortly) react immediately to a change in input, a glitch could initiate a cascade of undesirable transitions. Causing the system to perform poorly.
 - For an example, look at this (silly) system ...

 


Hazards (2)

- **Would this system work?**

 

 - You'd think the partygoers could breathe a sigh of relief, after all $(SW \cdot (((SW)')')')) = 0$. Right? Look at the timing diagram below.



Hazards (3)

- Although it might only last a few nanoseconds (transitions of 3 inverters), the glitch in the output *may* prove disastrous. **Steady state analysis is not indicative of dynamic performance.**
- This is a *static type 0 hazard*, where a change in the input which should see the output remain LOW determines a brief “1” glitch. There are also *type 1 hazards* (dual) and *dynamic hazards*.
 - See Wakerly 4.4
- Whether or not you need to worry about hazards depends on **how critical the impact of the glitch is on the output.**
- In sequential circuit design we can use **synchronisation** to neglect hazards. Signals are “sampled” at time intervals which are **far enough in time for all transient behaviour to have settled.**
 - You will see an example of this in CLAB 2

Summing up

- You now know about some non-ideal aspects of digital circuits with a particular focus on CMOS hardware:
 - Importance of correct voltages
 - For digital operation
 - To avoid excessive power dissipation
 - Role of loads in affecting timing
 - Hazards arising from propagation delays
- As you will learn to use computer-assisted design (CAD) tools, the software (ISE WebPACK in our lab activities) will assist you in diagnosing whether your design is at risk of undesirable behaviour.
 - Softwares are no substitute for a good understanding of the underlying principles. You need to have some idea of where to look when the CAD tools “complain” about your design.