

Week 3

Verilog HDL (continued)

Video Lecture 5

ENGN4213/6213
Digital Systems and Microprocessors

What's in this lecture

- Verilog HDL
 - More on blocking and nonblocking assignments
 - Procedural keywords and examples
 - Instantiations
 - Parameters
 - Timing specifications and test bench files
 - Examples

Resources

- Wakerly (5th edition) Chapter 5 for Verilog HDL
- Verilog code examples of combinational circuits can be found throughout Wakerly (5th edition) Chapters 6,7,8
- Verilog code examples of counters and shift registers can be found in Wakerly (5th edition) Chapter 11
- Many Verilog examples ready to compile and run with Icarus Verilog at the following website
<http://www.asic-world.com/examples/verilog/index.html>

Blocking vs Nonblocking assignments (again)

- *Review from last lecture*
- Two ways to assign values inside an **always** block
- **Blocking assignment**
 - Are “executed” at the end of each line.
 - The result of one assignment affects the next.
 - Normally used for combinational designs with *level sensitivity lists* [e.g., **always@ (<signal_names>), always@ (*)**]
- **Nonblocking assignments**
 - Are read in sequence but “executed” at the end of the **always** block.
 - The result of one assignment does not affect the next.
 - Normally used with *edge sensitivity list* [**always@ (posedge x)**]


Blocking vs Nonblocking assignments (2)

- Typical example

```
...
always @(posedge clk) begin
    a=b;
    b=a;
end
...
```




Relatively useless

 

```
...
always @(posedge clk) begin
    a<=b;
    b<=a;
end
...
```



Intended behaviour

 

Blocking vs Nonblocking assignments (3)

- **Basic rules are:**
 - **Blocking assignments** for **combinational** logic
 - **Nonblocking assignments** for **sequential** logic
- Other important rules
 - **Don't mix blocking and nonblocking** assignments in the same **always** block
 - Don't assign the same variable in multiple **always** blocks

Procedural keywords

- Used only inside always blocks
- Allows you to give a *behavioural description* of a circuit rather than a *structural* one
- Does look a lot like programming
 - But remember that your “program” must be synthesisable in hardware!

The `if ... else` keyword


- Some circuit event only occurs *if* a particular condition is verified, *else* some other event will take place
- Syntax

```
if (condition) begin
    <statement events if condition true>; end
else begin
    <statement events if condition false>;
end
```

- In **combinational designs**, you **must contemplate all *if* cases** in your code, otherwise the synthesiser may generate *inferred latches* (common mistake, also wastes hardware resources).
- **begin ... end** constructs are used if there are multiple statements within following *if* or *else*

 Example, the multiplexer

```
module MUX (  
    input wire X, S,  
    output reg Z);  
  
    always @ (*)  
        if (S==1) Z=X;  
        else Z=Y;  
endmodule
```



The case keyword


- **Similar to `if` (for conditional statements), but useful when there are *multiple cases*, not just a single T/F condition.**
- Syntax

```
case (case variable)
    value#1 : statement#1;
    value#2 : statement#2;
    ...
    default : statement if none of the above occur;
endcase
```

- **`begin ... end` constructs are used if there are multiple statements for any one case**
- We have already seen examples of this as very useful to do MUX, DEMUX and DECODERS

 Example: a bigger MUX (8-to-1)

```
module eight_to_1_MUX (  
    input wire [7:0] X,  
    input wire [2:0] sel,  
    output reg Y);  
  
    always @(*) begin: my_cases  
        case(sel)  
            3'd0 : Y = X[0];  
            3'd1 : Y = X[1];  
            3'd2 : Y = X[2];  
            3'd3 : Y = X[3];  
            3'd4 : Y = X[4];  
            3'd5 : Y = X[5];  
            3'd6 : Y = X[6];  
            3'd7 : Y = X[7];  
            default : Y=1'bx;  
        endcase  
    end  
endmodule
```



Looping statements: **for, while, repeat, forever**

- Carry out an operation over and over as long as
 - a looping index meets the requirements (**for**)
 - a counter is not exhausted (**repeat**)
 - a particular logical expression remains true (**while**)
 - the circuit is running (**forever**)

- Syntax

for (*index=initial; expression; index=next*)
procedural statements

repeat (*integer number of times*)
procedural statements

while (*logical expression*)
procedural statements

forever
procedural statements

Looping statements (2)

- **Looping statements are dangerous:**
 - They can create *non-synthesisable designs*
 - They often introduce *feedback*
 - Other times designs will *blow out in terms of hardware space requirements*
- **We will limit their use or avoid them altogether**
 - Not particularly useful for hardware designs. If anything, for sequential designs only
 - Somewhat *useful in writing test benches*
 - This is an important practical difference with computer programming, where loops are very common.

Examples with looping statements

- An example that chews up hardware

```
...  
always @ (*) begin  
    for (i=0; i<=63; i=i+1)  
        Y[i]=X[i]+i;  
end  
...
```

This will create **63 separate adders**
("unrolling" the loop)

- Non-synthesisable code

```
...  
always @ (*) begin  
    while (c<d) begin  
        c=c+2;  
        a=a+1;  
    end;  
end  
...
```

This module, which uses *a* to count how many +2 operations are required in order for *c* to become greater than *d*, **can't be synthesised** because the number of repetitions in the loop is unknown *a priori*, so the loop can't be "unrolled".

Examples with looping statements (2)

- An example that is useful in a testbench file

```
...  
forever begin  
    #1 sysclk=1;  
    #1 sysclk=0;  
end  
...
```

- This creates a signal `sysclk` which switches value between 0 and 1 at every time increment.
- This code *is not synthesisable* but it is useful to create a clock source for simulation purposes, for example.
- It uses timing specifications (that `#1`), which we will discuss shortly.

Instantiation

- The hierarchical nature of the Verilog language can be exploited by coding sub-modules separately and then calling upon them (***instantiating***) from a higher-level module. Let's refer to the calling module as the *master (m)* and the called module as the *slave (s)*
 - Instantiation is routine in simulations where the test bench file has the master role and the module under test is *an instance* of the slave
- **Instantiation syntax:**

```
module_name instance_name ( .s1(m1) , .s2(m2) , ... );
```

- Each slave module signal (*s#* stands for slave signal #) is listed preceded by a dot, while the corresponding signal in the master module is named in brackets (*m#* stands for master signal #).
 - **Paired signals need not have the same name**

Instantiation example

Slave module

```
module boolmod (
    input wire X, Y, W,
    output reg Z);


    always @(*)
        Z = (X & Y) | (X & W);

end
endmodule
```

Master module

```
module topmod (
    input wire A, B, C,
    output wire Z);
    wire D, E;
    boolmod mod1(.X(A), .Y(B),
        .W(C), .Z(D));
    boolmod mod2(.X(C), .Y(B),
        .W(D), .Z(E));

    assign Z = D & E;
endmodule
```

 

Parameters

- A clever tool to create modules which can be instantiated with varying bit-widths for inputs and outputs.
 - Saves time as it is not necessary to re-code the module each time
- **Syntax:**
 - Inside the module which will be instantiated
parameter *par_name = value;*
 - The parameter value inside the module declaration is the *default value* of the parameter
 - When instantiation is performed at master module level
module_name # (par_value) instance_name (i/o signals);
 - When used in an instantiation statement, the parameter value inside the # () placeholder will override the default parameter value for that particular instance only.

Parameterisation example

- A variable-width adder (default width 2 bits)

```
module cooladder (  
    input wire cin,  
    input wire [WID-1:0] X,  
    input wire [WID-1:0] Y,  
    output reg cout,  
    output reg [WID-1:0] Z);  
  
    parameter WID=2;  
    reg sum [WID:0];  
  
    always @(*) begin  
        sum = X+Y+cin;  
        Z=sum[WID-1:0];  
        cout=sum[WID];  
    end  
endmodule
```

- Three instantiations where a 2, 4 and 8-bit adders are instantiated

```
... //2-bit adder (default WID)  
cooladder add2 (.cin( ), .X( ),  
    .Y( ), .cout( ), .Z( ));  
...  
  
... //4-bit adder (WID=4)  
cooladder #(4) add4 (.cin( ),  
    .X( ), .Y( ), .cout( ), .Z( ));  
...  
  
... //8-bit adder (WID=8)  
cooladder #(8) add8 (.cin( ),  
    .X( ), .Y( ), .cout( ), .Z( ));  
...
```

Directives

- High-level commands which inform compilation
 - **``include "filename"`**
 - The named file is read and processed as part of the file containing the directive. It is a convenient way to refer programmatically to module definitions located in different folders.
 - **``define identifier text`**
 - Used to rename things. Every time *identifier* is used in the code, it will be replaced by text. I could, for example, rename the net type *wire [3:0]* to *bus4*.
 - **``timescale ts / tp`**
 - Used to specify the time step (*ts*) and precision (*tp*) to be adopted
NOTE: this can be used in simulations only!

System tasks


- A number of predefined system tasks affect the behaviour of the simulator. There are many. Only a handful of useful ones are listed here. We will use some in test benches.
 - **\$dumpfile** (*"filename"*) is used to specify the name of the file in which the simulation results will be saved (generally a .vcd file)
 - **\$dumpvars** (*mode*, *list_of_variables_or_modules*) ; specifies that changes in the variables need to be saved in the dump file
 - *mode* and *list* are optional. If *mode* is 0, all variables of the listed modules will be dumped; if 1, only the listed variables from the listed modules will be dumped.
 - **\$display**(*string*) ; can be used to print a text-based output in the terminal console as the simulation is running
 - the format of the string is given in C-language-like syntax.
 - **\$monitor**(*string*) ; like \$display but always active so prints the output at every signal change.
 - **\$finish** forces a simulation to terminate

Timing specifications

- Can be used to specify time delays in circuit operations
 - Time delay specifications are ***not synthesisable***
 - They are commonly used in test benches
- **Syntax:**
 - Basic construct: `#X` where `X` is to be replaced by the required number of time delay steps
 - Remember: the length of a time step is specified by ``timescale`
 - Depending on where the construct is placed in a statement, different timing effects can be achieved. The most common:
 - **wire** `#10 A;` all assignments which affect `A` will only take effect after 10 time steps
 - **assign** `#5 a = b+c;` the value of `b+c` is evaluated instantly but assigned to `a` after 5 time steps
 - *inside procedural blocks* `#7 q = x+y;` executes the assignment after 7 time steps

Test benches

 - A test bench is a top module with no external inputs or outputs
- It is only valuable for simulation
- It provides a description of test signals which will be fed to the inputs of a design under test and lists the test outputs which will be read (UUT= Unit Under Test)



Test benches: typical structure

Essential test bench structure (code very similar to CLAB1)

```
`timescale 1ns / 1ps //specifies simulation time steps (default 1ns)
module TB_mux1;      //A TB is a normal module, just with no i/o
    reg X;
    reg S;           //Inputs: note they are of type reg
    reg Y;
    wire Z;          //Outputs: note they are of type wire

    mux mx(.X(X), .S(S), .Y(Y), .Z(Z)); //instantiation of module under test

    initial begin
        $dumpfile ("mux.vcd");          //dumpfile name specification
        $dumpvars;                       //activate variable change dump (all)
        #20; $finish;                   //specifies simulation duration (20ns)
    end

    initial begin
        #1X = 1'b0;
        #1Y = 1'b1;
        #1S = 1'b1;                      //procedural block (initial) to specify signal changes
        ...
        #1Y = 1'b0;
        #1S = 1'b0;
    end
end
endmodule
```


The `initial` block

- It is a procedural block, so it can contain procedural statements like the `always` block.
- It's generally **not synthesisable** (there are exceptions)
 - **Only used in simulation** modules
- Unlike `always`, it has no associated sensitivity list.
 - the code is **executed *at the beginning*** of the simulation (at time 0)
- It is ok to have multiple initial blocks
- The `begin ... end` construct can be used when multiple lines of procedural code are required

Concluding remarks

- This concludes our **quick overview** of Verilog HDL fundamentals
- There are a number of more complex advanced features which we have not discussed, but **what we have covered is sufficient to carry out moderately complex designs**.
- I recommend you **limit yourselves to learning these essentials** for the purpose of the course (to avoid confusion).
- The best way forward is to **write your own code and study already written examples** (plenty of them in your textbook).
- **The very essential things to remember:**
 - Verilog can do both **simulation and synthesis**, and **some constructs which work in simulations do not work in synthesis**
 - There are **general rules on how to do sequential and combinational designs**. Although they are not absolutes, **if you follow them you should be able to avoid common mistakes**.

The key coding rules: Verilog for synthesis

General rules

- No `initial` blocks
- Avoid looping statements whenever possible
 - Think that the synthesiser will work only if it can “unroll the loop”
- No delay specifications
- Specify the bit width of all numbers you use.
 - It’s good practice and avoids involuntary hardware wastage
 - Example: `a[3:0] = b[3:0] + 8;` ***is 8 a 32-bit integer (default)?*
viz: `a[3:0] = b[3:0] + 4'd8;`
- In conditional statements prefer **case** to nested **if/else** if there are multiple cases to prevent the synthesis of slow gate chains in hardware.

The key coding rules: **combinational logic**

- Value assignments inside the design module must be done with **all inputs on the RHS, and all outputs on the LHS**
- **No feedback loops** permitted (follows from the previous rule)
- Use **continuous assignment** `assign` for simple comb. logic
- Use a **level sensitivity list** `always @ (*)` for procedural blocks
- Use **only blocking assignments** `"=`
- **If statements must be complete**, i.e., all variables changed within an `if` statement should have a value assigned to them regardless of whether the conditional clause is true or false (use of `else` or resort to default cases). This is to ***avoid inferred latches***.

The key coding rules: **sequential logic**

- Use an **edge sensitivity list** with a single clock entry, e.g., `always @ (posedge sysclk)`
- Use only **non-blocking assignments** "`<=`"
- The clock triggers the execution of procedural blocks, but **the clock does not appear inside the block**
- **If statements do not need to be complete**
- **Feedback loops are fine**
- Any **external signals must be synchronised** (to avoid metastability)

Examples



• The T-Flip flop

```

module tff(
  input wire CK,
  input wire EN,
  output reg Q);
  always @(posedge CK) begin
    if (EN) Q <= ~Q;
  end
endmodule

```


Note possible
alternative
symbol

  

 Examples (2)

- An 8-bit up-counter with enable and reset


```
module counter8(  
  input wire CLK, RST, EN,  
  output reg [7:0] count);  
  always @(posedge CLK) begin  
    if(reset) count <= 8'h00;  
    else  
      if(EN) count <= count + 1'b1;  
    end  
  end  
endmodule
```



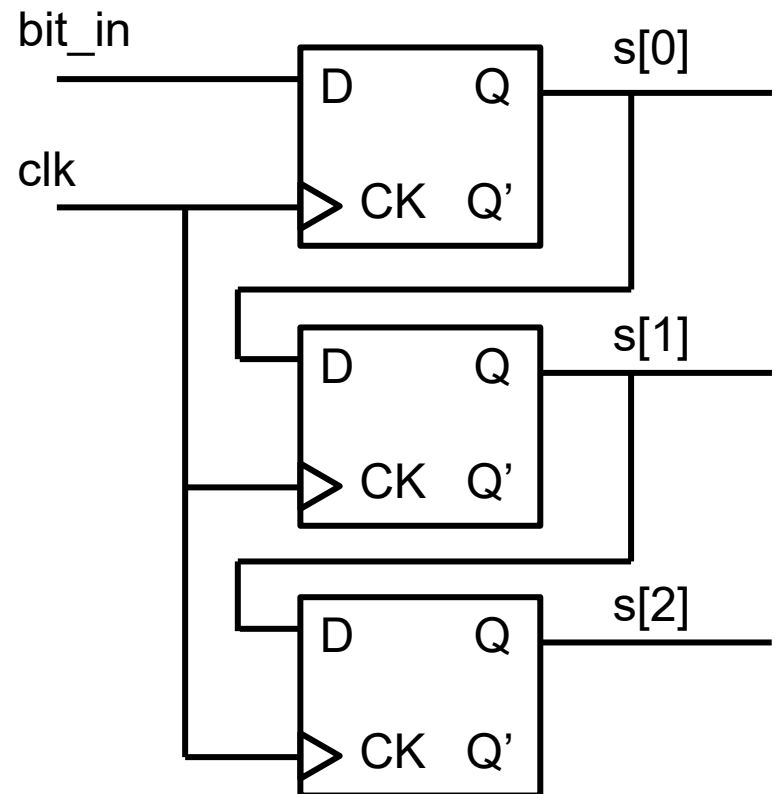Examples (3)

- A 3-bit SIPO (serial-in parallel-out) shift register

```
module siporeg(  
  input wire clk, reset, bit_in,  
  output reg [2:0] s);  
  
  always @(posedge clk) begin  
    if(reset)  
      s <= 3'b000;  
    else begin  
      s[0] <= bit_in;  
      s[1] <= s[0];  
      s[2] <= s[1];  
    end  
  end  
endmodule
```



Example (4)


- An 8-bit “one-hot” counter

```

module one_hot_cnt8 (
input wire en, clk, rst,
output reg [7:0] out);

always @ (posedge clk)
    if (rst) begin
        out <= 8'b00000001 ;
    end else if (en) begin
        out <= {out[6],out[5],out[4],out[3],
                out[2],out[1],out[0],out[7]};
    end
endmodule

```

 

Summing up

- We have completed a full overview of the **main features of Verilog HDL**. Today's lecture introduced
 - Procedural statements
 - Instantiations
 - Timing specifications
 - Test bench files and their typical structure
- We have learned that the language can be used for circuit **simulation** and **synthesis**
 - The two uses have **some differences** in the way the code is written
 - There are **good coding practices** for **combinational** and **sequential** logic designs
- We have commented on a few significant examples
 - Now it is up to you to master the language through **practice, practice, practice**.