

Week 4

Finite-State Machines

Video Lecture

ENGN4213/6213

Digital Systems and Microprocessors

What's in this lecture

- Finite-State Machine (FSM) concepts and definitions
- Representation of state machines
- Designing state machines

Resources

- Wakerly (5 edition) Ch.9: introduction to some general concepts and definitions
 - Wakerly Ch. 9.1-9.2 for analysis of state machines
 - Wakerly Ch. 9.3 for FSM design with state tables
 - Wakerly Ch. 9.4 for FSM design with state diagrams
 - Wakerly Ch. 9.6 for FSM design with Verilog
- Wakerly (5 edition) Ch.12 for FSM design with examples
 - Wakerly Ch. 12.7 for an example of a FSM machine implementing a “guessing game”
 - (not strictly required: read it if it helps your understanding)
 - Wakerly Ch.12.9 for decomposing state machines


The concept of *state*

- We have already learned that in a *sequential circuit*, the output (y) is a function (f_s) of current and past inputs (u)
- This is opposed to *combinational circuits*, where inputs and outputs are related through a boolean function of some sort (f_c) (*truth table*).
- Mathematically, this could be written as
 - For a combinational circuit $y(t)=f_c(u(t))$
 - For a sequential circuit $y(t)=f_s(u(t),u(t-1),u(t-2),\dots)$
- But how many time steps of input history are required to describe a system completely?
 - This may vary depending on the system.
 - For some systems a full input history might be required, making for a rather intractable description

The concept of *state* (2)

 - **Example:**

- consider a counter circuit: every time a push button is pressed the counter is incremented by 1.



- the output of such a system depends on the full history of inputs (how many times the button has been pushed). Also, since the timing of the button pushes is unknown, how can f_s be established unambiguously?
- A better way of describing sequential systems is required. That's where the concept of *state* becomes useful.

The concept of *state* (3)

- Your textbook (Ch.9) gives a very good **definition** of the concept of *state*:

The state of a sequential circuit is a collection of state variables whose values at any time contain all the information about the past necessary to account for the circuit's future behaviour.

- In the counter example, a valid state variable s is the value of the count. The output can be unambiguously described as a function of the current count and input: $y(t) = f_s(s(t), u(t)) = s(t) + u(t)$

The concept of *state* (4)

- You have already encountered the concept of state in your earlier studies if you have learned about ***dynamical systems***. You will most likely know of state-space models. For a linear discrete-time dynamical system a common formulation is:

$$\mathbf{s}(t+1) = \mathbf{A}\mathbf{s}(t) + \mathbf{B}\mathbf{u}(t) \quad \textit{next state equation}$$

$$\mathbf{y}(t) = \mathbf{C}\mathbf{s}(t) + \mathbf{D}\mathbf{u}(t) \quad \textit{output equation}$$


- Indeed, we will use “next-state” concepts in our treatment of sequential circuits. A sequential circuit ***is*** a dynamical system (although not necessarily a linear system).

Finite-State Machines

- In a sequential logic circuit, the state variables are **binary variables**.
 - it means that a circuit with n state variables will have 2^n possible states
- In sequential circuits the number of variables can be large but is finite. Hence the name ***finite-state machine***.
 - All sequential logic circuits can be interpreted as FSM
 - As your textbook suggests it is possible to make a theoretical case for a non-finite-state machine (e.g. a Turing machine), but for this course we are interested in practical, finite-state designs.

Clock signals (synchronous systems)

 - We have already talked about these, just a few more specifications:



- Clock period = t_{per} , frequency = $1 / t_{per}$
- For a synchronous system driven by an “**active high**” clock:
 - **State transitions** occur at **rising** clock edges (\uparrow)
 - The **duty cycle** of the clock is calculated as t_H / t_{per}
- For a synchronous system driven by an “**active low**” clock:
 - **State transitions** occur at **falling** clock edges (\downarrow)
 - The **duty cycle** of the clock is calculated as t_L / t_{per}

State-machine description

- **Mathematical description**

- **Mealy machines**

- The output at time t depends on both the state and input at time t

$$s(t+1) = F(s(t), u(t)) \quad \text{next state equation}$$

$$y(t) = G(s(t), u(t)) \quad \text{output equation}$$

- **Moore machines**


- The output at time t depends only on the state at time t

$$s(t+1) = F(s(t), u(t)) \quad \text{next state equation}$$

$$y(t) = G(s(t)) \quad \text{output equation}$$


State-machine description (2)

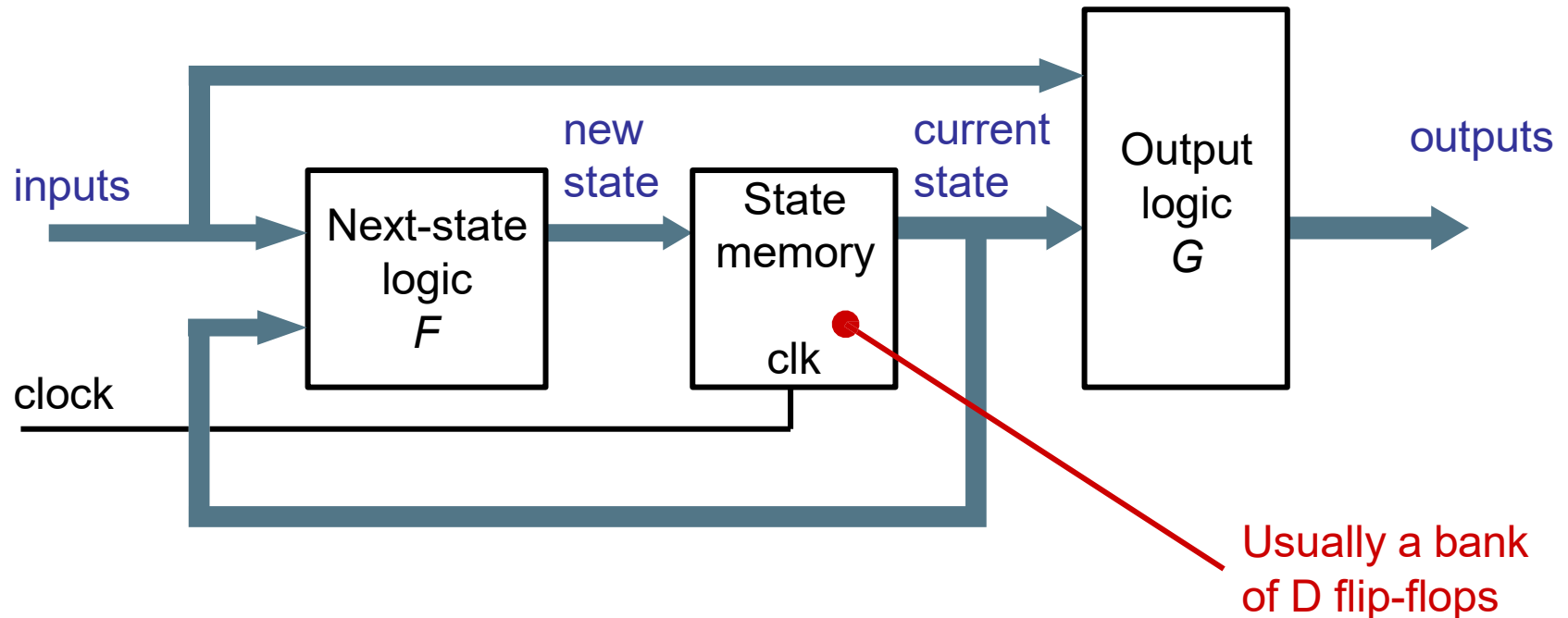- **Block-Diagram representation**
 - **Mealy machines**



State-machine description (3)

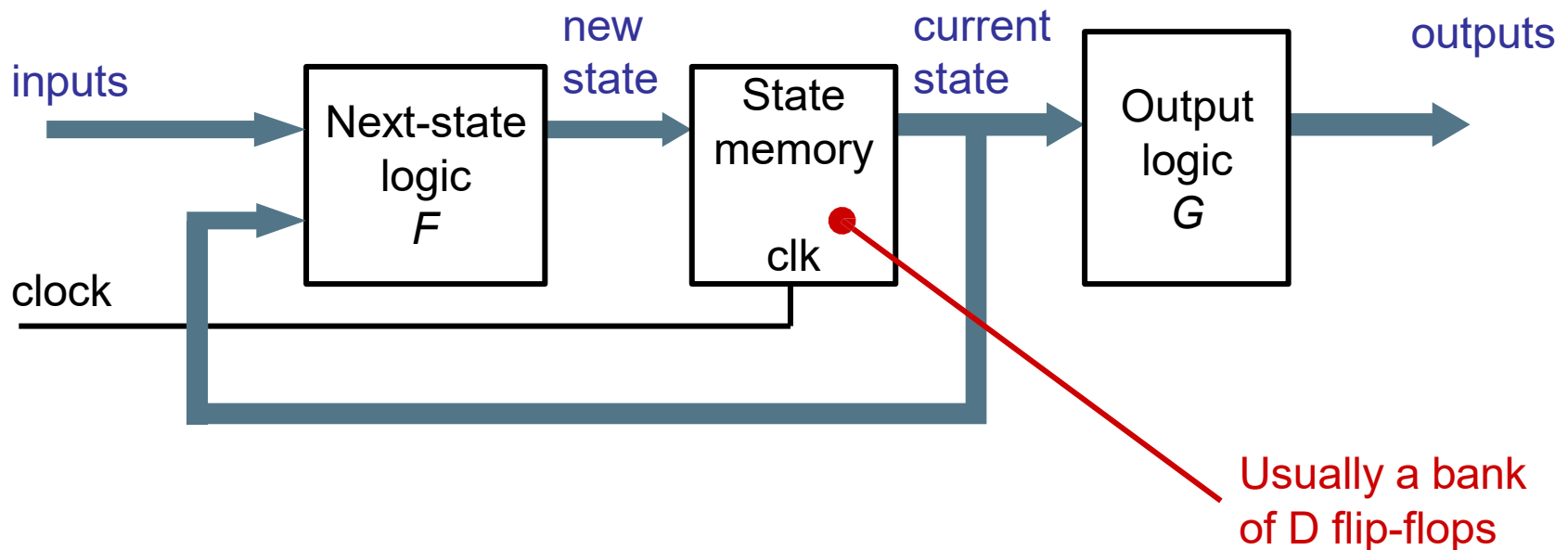- **Block-Diagram representation**
 - **Moore machines**



Finite state machine structure

- The **state memory** is the true sequential part of a design. Generally implemented as n flip flops for 2^n states. (*why?*)
- The flip-flops undergo their transitions (change of state) on the active edge of a common clock – **synchronous state machine**
- The next state is determined by the **next state logic F** which is a function of the inputs and the current state.
- The **output logic G** determines the output as a function of the current state and (Mealy machine) the inputs.
- Thus we see that a **synchronous FSM consists of two combinational blocks** (the input and output logic blocks) **and one sequential block** (the state memory block)



State diagrams

- **A way to represent the FSM in one diagram**
 - **States** are symbolised by a **bubble** in the form of a circle or a box.
 - **Loops or branches** between the state bubbles represent **state transitions** with the input condition for the transition written on them
 - For a *Mealy machine* the outputs depend on both the input and the state. Thus they are written underneath the inputs on the loops
 - The outputs of a *Moore machine* can be written inside the state bubbles

State diagrams (2)

- Example:**
a 2-bit counter (state=current count)

A Moore or Mealy machine?

  

Tables

- A FSM machine can also be described using tables:
 - **transition tables**,
 - **state tables**
 - **state/output tables**
- **Transition tables** represent the relationship between the current state value and next state value as a function of the input
- **State tables** are very similar but more intuitive for complex states as the states are assigned a mnemonic description
- **State/output tables** also include the relationship between the state and the output. These can become complicated for Mealy machines as the output is also a function of the input.
- You can draw one or more of these tables, or condense them together as one single *input | next state | output* table.


Tables (2)

- The counter example (again):**

Transition table			State table			State/output table	
State value S	Input C		State name	Input C		State name	Output OUT
	0	1		0	1		
00	00	01	s0	s0	s1	s0	00
01	01	10	s1	s1	s2	s1	01
10	10	11	s2	s2	s3	s2	10
11	11	00	s3	s3	s0	s3	11
Next state S*			Next state				

- Note:** the notation S^* indicates the value of S “at the next time step” (next clock cycle).

Schematic representation of a FSM

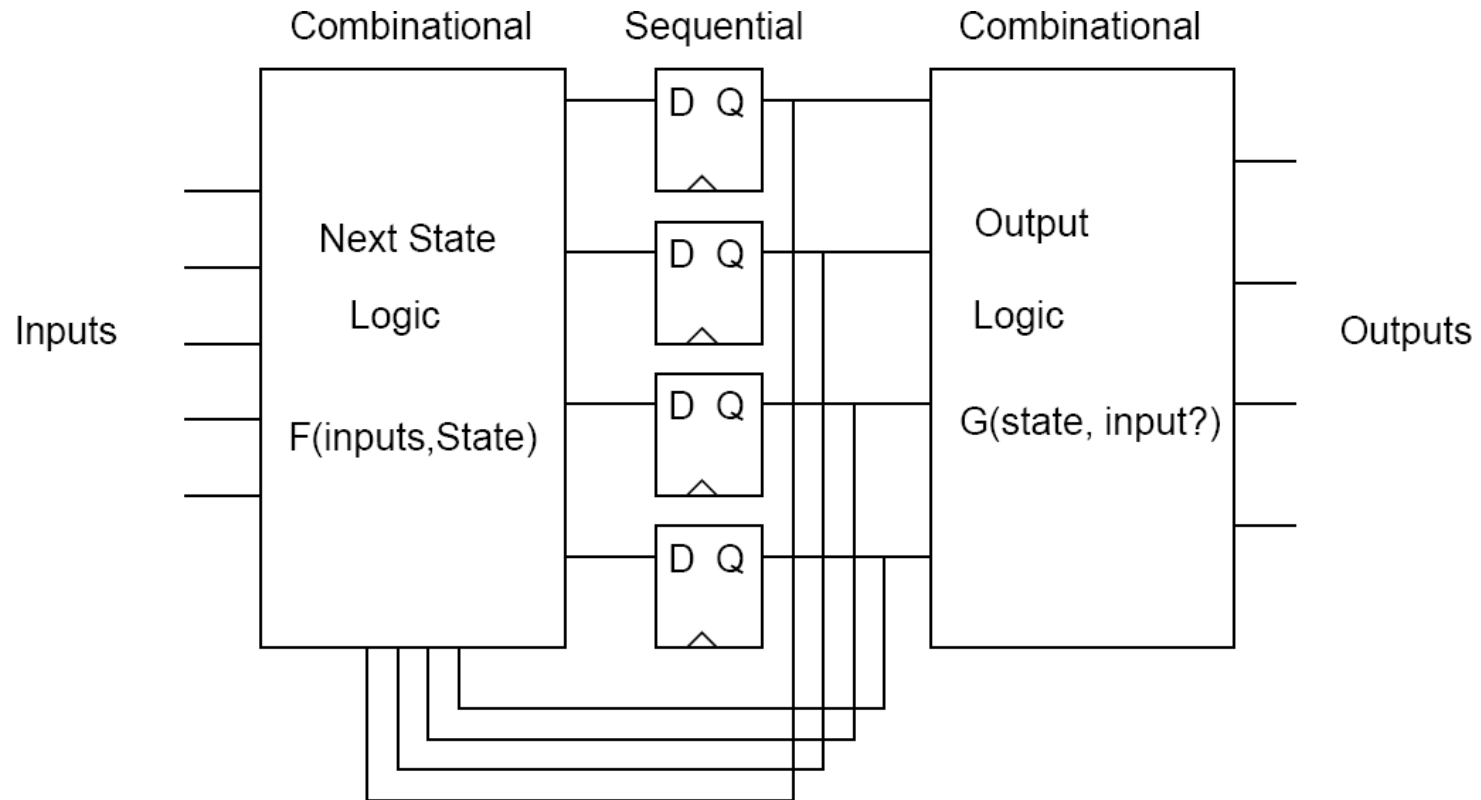

Finite-state machines in Verilog

- The transition between states is a sequential operation (in the sense of a **sequential circuit**)
- In a FSM the actions that produce outputs from the inputs are always **combinational**
- From a coding perspective
- For state transitions, use a **sequential always block**
- For next state logic, use a **combinational always block**
- For output logic, use a **combinational always block** or **assign statements**

Two-state *Moore* machine in Verilog

```
module FSM
(input wire clk, rst, input,
output reg out);
parameter S0 = 1'b0, S1 = 1'b1;
reg state, Snext;
always @(posedge clk)
//STATE MEMORY - SEQUENTIAL
if(rst)
state <= S0;
else state <= Snext;

always @(*) begin
//NEXT STATE LOGIC -COMBINAT.
case(state)
S0: if(input) Snext = S1;
else Snext = S0;
S1: if(input) Snext = S0;
else Snext = S1;
```

```
default: Snext = S0;
endcase
end

always @(*) begin
//OUTPUT LOGIC -COMBINAT
case(state)
S0: out = f(state);
S1: out = g(state);
default: out = h(state);
//note: f,g,h arbitrary
endcase
end

endmodule
```

Two-state *Mealy* machine in Verilog

```
module FSM
(input wire clk, rst, input,
output reg out);
parameter S0 = 1'b0, S1 = 1'b1;
reg state, Snext;
always @(posedge clk)
//STATE MEMORY - SEQUENTIAL
if(rst)
state <= S0;
else state <= Snext;

always @(*) begin
//NEXT STATE LOGIC -COMBINAT.
case(state)
S0: if(input) Snext = S1;
    else Snext = S0;
S1: if(input) Snext = S0;
    else Snext = S1;

    default: Snext = S0;
endcase
end

always @(*) begin
//OUTPUT LOGIC -COMBINAT
case(state)
S0: out = f(input,state);
S1: out = g(input,state);
default:
out = h(input,state);
//note: f,g,h arbitrary
endcase
end
endmodule
```

Designing a FSM – the key steps

1. Determine the inputs / outputs. **Determine the states and give them mnemonic names**
2. Draw up a state diagram and a next state table.
3. Render the inputs and outputs in binary format, adopt an encoding for the states (you can use Verilog **parameter** to your advantage).
4. Draw a **transition table (next-state value table)**
5. Draw an **output table**
6. Use Boolean algebra (Karnaugh maps where practical) to obtain **minimal next state and output combinational logic**.
7. Use the standard Verilog style to **code and simulate your design** and check for correct operation. Revise as appropriate.
8. Check for potential practical problems (e.g. non-ideal effects).

Determining the states

- Usually a design is described in terms of:
“I want a system that takes in such and such inputs and does something (outputs) when something else (input sequence) happens.”
 - This can be turned into a state-based description using state tables and/or state diagrams.
 - State tables are more precise but state diagrams are often more intuitive
- You should try to come up with **as few states as possible**:
 - Saving resources / easier to manage designs
 - **Equivalent states**, i.e., states associated with the same output and the same next-state transitions can be replaced by a single state.
- Use **meaningful names**!
- Once you have picked the states the number of required flip-flops is automatically derived


Assigning binary coding to the states

General rules to assign binary values to the states:

 1. Choose an initial state which is easy to initialise (00..0)
2. Minimize the number of bit changes between adjacent states (Grey code can help)
3. Exploit symmetries: if a state or group of states are very similarly related, they can be assigned the same code with the exception of 1 bit.
4. If you have unused states, make use of the full range of binary numbers in order to achieve the above as much as possible
 - e.g., if you have 5 states (3 bits), don't stop at 101.
5. If each bit (or subgroup of bits) has a meaning, exploiting these meanings can lead to simpler next-state logic.

Designing good transition and output logic

- Karnaugh maps are a good tool when working with simple designs
 - See your textbook for an example of K-maps for more than 4 variables
- When transition/output equations are complicated you can simplify the expressions using Boolean algebra to some extent.
 - But it might be hard to come up with a minimal description
 - CAD tools (synthesisers in particular) do take some of the trouble out of this by carrying out their own complexity reduction algorithms.
- If you are working with state diagrams ensure that your diagram has no ambiguity before working on the transition logic!
 - Ambiguity can arise when different inputs can cause the system to evolve to different states.
But what happens if both inputs are asserted at once?



What if both
A and B are 1?
Disambiguation
required!

Summing up

- We have introduced **finite-state machine** concepts:
 - the concept of *state* and how it describes a system's dynamic behaviour
 - Mealy and Moore state machines
- We have seen how to describe state machines:
 - In terms of **state diagrams**
 - In terms of **tables (state, transition, output)**
- We have laid out some basic steps for FSM design
- All will be much clearer with real examples