



ENGN 4213/6213 Digital Systems and Microprocessors
Semester 1, 2023

Tutorial 3

Question 1:

Consider the following Verilog code when answering Question 1:

```
module mymod(  
    input wire a,  
    input wire b,  
    input wire f,  
    input wire [3:0] e,  
    output wire c);  
  
    reg [3:0] d;  
  
    always @(posedge b) begin  
        if(a) d <= e;  
        else if(f) d <= {1'b0, d[3:1]};  
    end  
  
    assign c = d[0];  
  
endmodule
```

- Draw a block diagram detailed to flip-flop level
- Explain the functional role of entities a, b, c, d, e and f
- Suggest a possible use for the behaviour of this module
- Is this design sequential or combinational? Explain your answer
- Is this design synchronous or asynchronous? Explain your answer

Question 2:

You wish to design a circuit with one button and four LEDs such that one LED is on at once, and each press of the button turns the next on the next LED in sequence:

 


Figure 1

- What is the name of this type of counter?
- Sketch the logic that might be used to implement this behaviour
- The output of this circuit can be used as a 'selector' for down-stream behaviour.
Write a short combinatorial Verilog snippet that takes the outputs of this counter as inputs, and has the following outputs itself:
 - A 16-bit bus called *A*
 - An 8-bit bus called *D*
 - A one-bit line called *LA*
 - A one-bit line called *RW*

 


Figure 2

The Verilog code should represent a design which does the following in order:

First state: Set *A* to '143' (the rest should be '0')

Second state: Set *LA* to '1'

Third state: Set *D* to '42', *RW* to '1', *LA* to '0'

Fourth state: Set *RW* to '0'

Congratulations, you just wrote your first state machine! This example would be suitable for storing the value '42' at address '143' in some external RAM.